

Lab 5 & 6: Assignment 1 (10 Marks)

Date for Showing the output to Instructor (No Deduction): 17/09/2021 between 11AM-1PM

Due Date for final submission through CMS: 17/09/2021 9:00 PM

Name: Lakshmi Mounika Chaturvedula

ID No: 2019A8PS0621H

Problem Statement: Design a state machine to control the tail lights of a 1965 Ford Thunder bird (Figure 1). The tail lights are composed of three lights on each side which operate for the turns as shown in figure 2. The state machine has two inputs (**LEFT**, **RIGHT**) and 6 outputs (**LC**, **LB**, **LA**, **RA**, **RB** and **RC**). When (**RIGHT=0** and **LEFT=0**) or when (**RIGHT=1** and **LEFT=1**) no lights will turn ON. If (**RIGHT=0** and **LEFT=1**) then lights **LC**, **LB**, and **LA** will be ON as shown in figure 2(a) indicating **LEFT** turn. If (**RIGHT=1** and **LEFT=0**) then lights **RA**, **RB**, and **RC** will be ON as shown in figure 2(b) indicating **RIGHT** turn. In addition to **LEFT** and **RIGHT** there are two more inputs **Clk** and **Reset** for normal operation of FSM. When **Reset** is enabled all lights will be OFF. The flashing rate of LEDs is 2Hz (i.e. the time between two successive states is 0.5s).

PIN Assignment:

Inputs: **RIGHT** → F22; **LEFT** → G22;

Outputs: **LC** → U14; **LB** → U19; **LA** → W22; **RA** → U22; **RB** → T21; **RC** → T22;

 


Figure 1

 


Figure 2(a)

Figure 2(b)

Figure 2

(Please refer to the file named “Vivado_Design_Flow_All_Steps.pdf” for a review of all the steps

in the design flow)

1. Question: Draw the FSM (can be an image) with proper description.

Answer:

1) Given, inputs- clk, reset, left, right
outputs- 6 o/p (3 for left & 3 for right)

Let the parameters/state encodings be S0-000 - All lights off

State diagram:

S1-001 - LA on (as per assignment)

S2-010 - LA, LB on

S3-011 - LA, LB, LC on


S4-100 - RA on (as per assignment)

S5-101 - RA, RB on

S6-110 - RA, RB, RC on

Can't happen ← [S7-111 - LA, LB, LC, RA, RB, RC ON (whose o/p should be directed to 000000)]

State Transition Diagram:

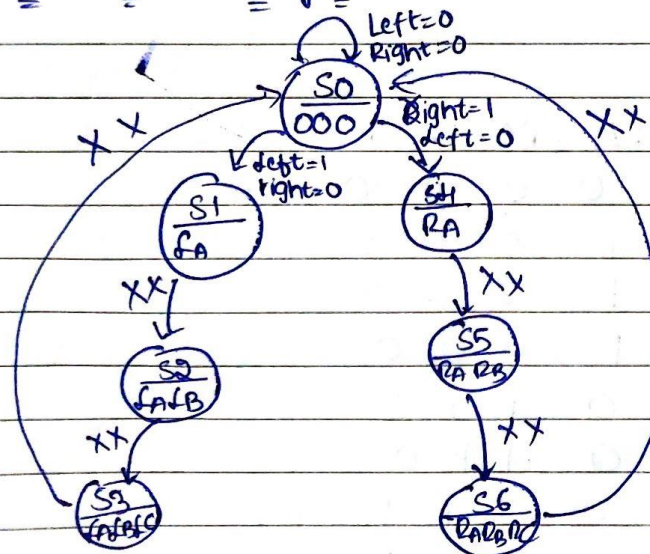


Left = left (i/p)
Right = right (i/p)

Page No.

State Transition Table (with the encodings):

Present State	Input left	Input right	Next State	Output out left, a, b, c
S0 (000)	0	0	S0 (000)	0 0 0 0 0 0
S0 (000)	1	0	S1 (001)	0 0 1 0 0 0
S1 (001)	X	X	S2 (010)	0 1 1 0 0 0
S2 (010)	X	X	S3 (011)	1 1 1 0 0 0
S3 (011)	X	X	S0 (000)	0 0 0 0 0 0
S0 (000)	0	1	S4 (100)	0 0 0 1 0 0
S4 (100)	X	X	S5 (101)	0 0 0 1 1 0
S5 (101)	X	X	S6 (110)	0 0 0 1 1 1
S6 (110)	X	X	S0 (000)	0 0 0 0 0 0

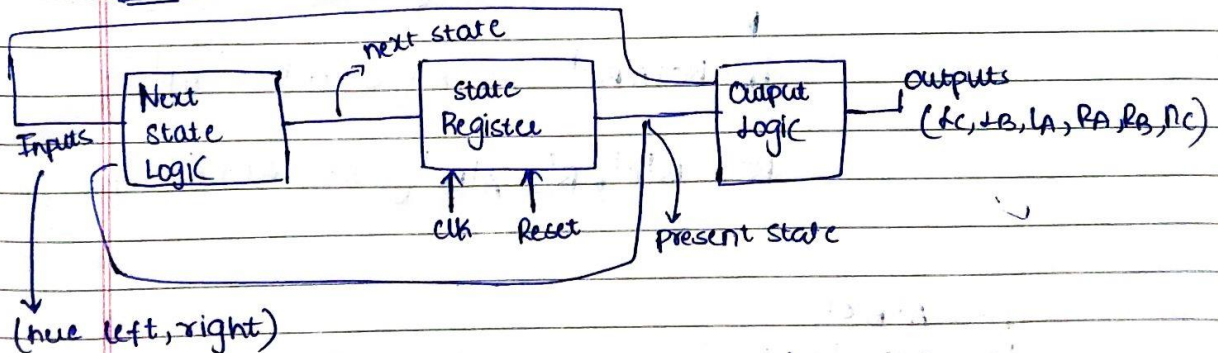FSM:

* The description for next state, present state is mentioned in the table

* If $Reset = 1$ then present state is S0
 ↓
 (positive edge only) else present state is next state

* Even the clock is taken as the posedge (clock) into verilog code

Date ___/___/___

Saathi

* We can use D flipflops to do for next states & output.

So, D flipflop inputs will simply be next state values i.e.,

(ABC) Present state	(d) Input (left)	(R) Input (right)	(ABC) Next state	D flipflop/p D _A D _B D _C	Output L _C L _B L _A R _A R _B R _C
000	00	0	000	000	000 000
000	0	1	100	100	000 100
000	1	0	001	001	000 000
000	X	X	000	000	000000
001	X	X	010	010	011000
010	X	X	011	011	111000
011	X	X	000	000	000000
100	X	X	101	101	000110
101	X	X	110	110	000111
110	X	X	000	000	000000

and any other state of - 000000

For Next states $\Rightarrow D_A = AB'C + B'C'L'R$ ($\because A'B'C' \downarrow R + ABC'L'R + AB'C$)

$$D_B = B'C + A'BC' \quad (\because A'B'C + A'BC' + AB'C)$$

$$D_C = B'C'L'R + A'BC' \quad (\because A'B'C'L'R + A'BC' + AB'C'L'R)$$

from don't care

$$L_C = A'BC'$$

$$L_B = A'BC' + A'BC$$

$$L_A = A'BC' + A'B'C + A'B'C'L'R' \\ = A'BC' + A'B'[(C+C')(C+R')]]$$

Similarly


$$R_C = AB'C$$

$$R_B = AB'C + AB'C' = AB'$$

$$R_A = AB'C + AB'C' + A'B'C'L'R \\ = AB' + A'B'C'L'R$$

Date: / /

Representation of FSM using D-FF

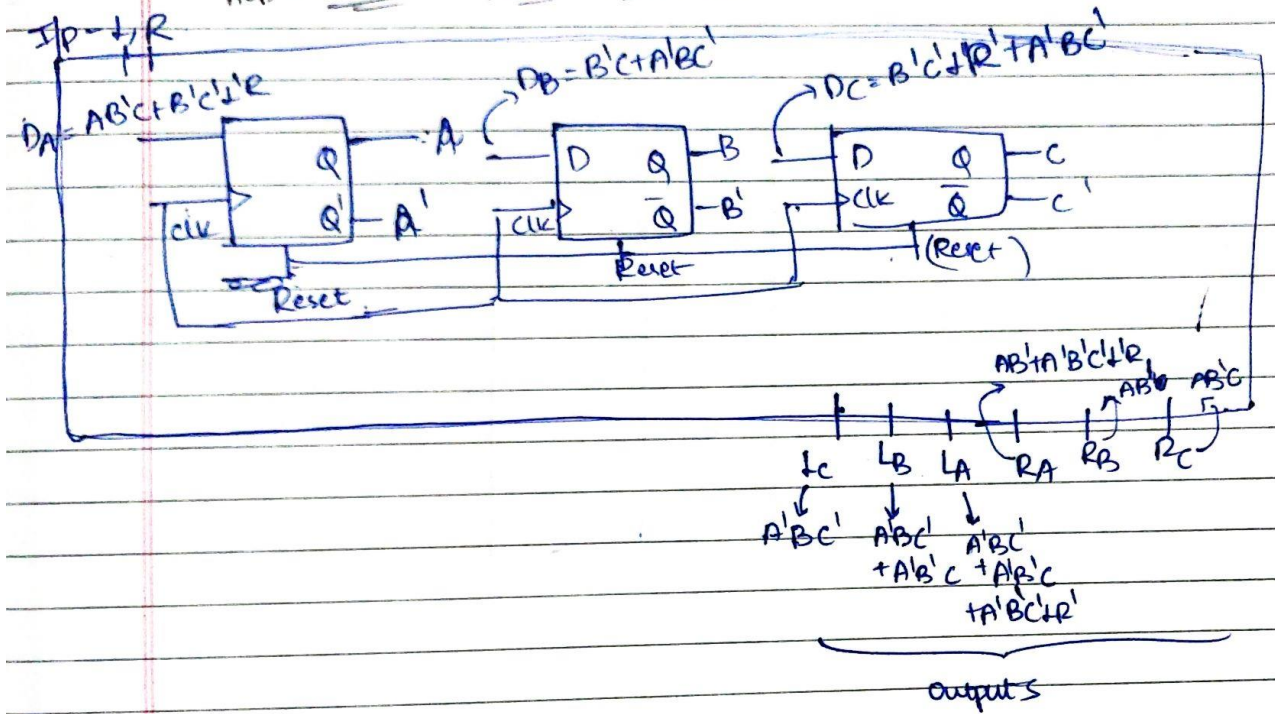

2. Create a Vivado Project and write Verilog code (Car_FSM.v with comments) for implementing

the above FSM.

Question: Paste the image of verilog code Car_FSM.v.

Answer: Without the clock division

```
module Car_FSM(  
    input left,right,//for left and right lights  
    input Clk,  
    input Reset,  
    output reg [5:0] out//light outputs  
);  
    //define present state and next state in the state diagram  
    reg[2:0] next_state,present_state;  
    //Use the keyword parameter for defining the state variables  
    //these are choosen as a reference for defining present state, next state  
    parameter S0=3'b000,  
               S1=3'b001,  
               S2=3'b010,  
               S3=3'b011,  
               S4=3'b100,  
               S5=3'b101,  
               S6=3'b110;  
    //Impelmentation of FSM----->State Register without clk_dividion  
    //reg [25:0] Clk_Div;  
    //always@(posedge Clk,posedge Reset)  
    // begin  
    // if(Reset==1)  
    //   Clk_Div=0;  
    // else  
    //   Clk_Div=Clk_Div+1;  
    //end
```

```

always@(posedge Clk, posedge Reset)
begin
if(Reset==1)
present_state=3'b000; //Present State will be zero if the reset is high
else
present_state=next_state;
end
//Input and Output Logic.....
//Input+Next state logic
always@(present_state[2:0],left,right)
begin
case(present_state)
S0:begin//From S0 the lights can go either in left and right direction and they are mentioned below
if(left==0 && right==0)
next_state=S0;
else if(left==1 && right!=1)
next_state=S1;
else if(right==1 && left!=1)
next_state=S4;
else
next_state=S0;
end
S1:next_state=S2;
S2:next_state=S3;
S3:next_state=S0;
S4:next_state=S5;
S5:next_state=S6;
S6:next_state=S0;
default: next_state=S0;
endcase
end
//Output Block implementation.....
always@(present_state[2:0],left,right) //Output also depends on the left and right
begin
case(present_state[2:0])
S0:begin
if(left==0 && right==0)
out=6'b000000;
else if(left==1 && right!=1) //left side light starts to glow
out=6'b001000;
else if(right==1 && left!=1) //right side light starts to glow
out=6'b000100;
else
out=6'b000000;
end
S1:out=6'b011000;
S2:out=6'b111000;
S3:out=6'b000000;
S4:out=6'b000110;
S5:out=6'b000111;
S6:out=6'b000000;
default: out=6'b000000;
endcase
end
endmodule

```

3. Write the test bench **Test_Car_FSM.v** and simulate your design to check the functionality.


Question: Paste the image of test bench verilog code Test_Car_FSM.v.

Answer:


```
module Test_Car_FSM(  
    );  
    reg left,right;  
    reg Clk,Reset;  
    wire [5:0] out;  
    Car_FSM cl(left,right, Clk, Reset, out);  
    //Generation of Clock  
    initial begin  
        Clk=1'b0;  
        repeat(32)  
            #5 Clk=~Clk;  
    $finish;  
    end  
    //Generation of Reset  
    initial begin  
        Reset=1'b1;//Reset is set to 1  
        #9  
        Reset=1'b0;//Reset is set to 0  
    end  
    //Generation of Lights  
    initial begin  
        #40//For left side lights  
        left=1;  
        right=0;  
        #30//For right side lights  
        right=1;  
        left=0;  
    end  
endmodule
```

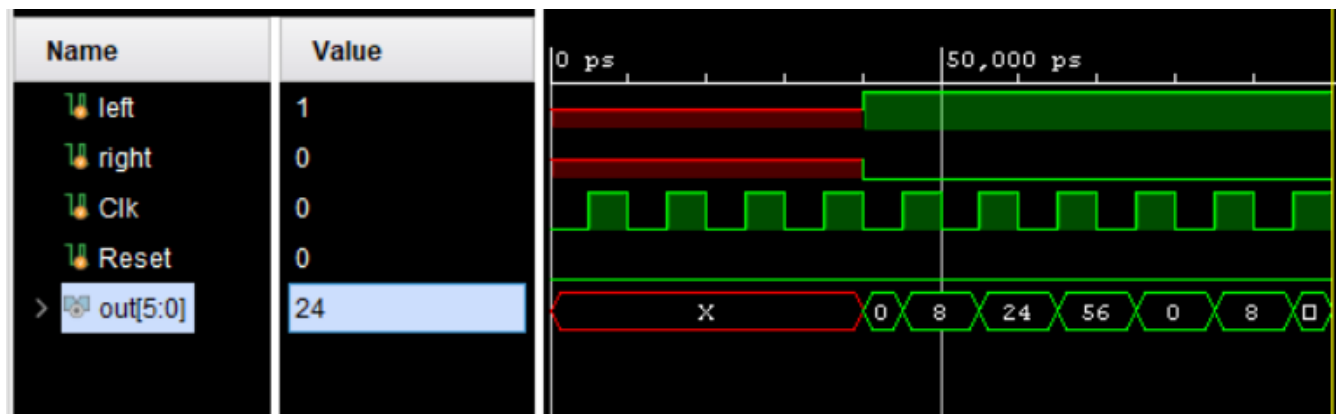Question: Paste the image showing the simulated waveforms for FSM (Behavioral Simulation). Clearly show the LEFT turn and RIGHT turn Cases.

Answer: LEFT TURN: 0001000-8; 011000-24; 111000-56 (Put Left=1 and Right=0 in the Test Bench)



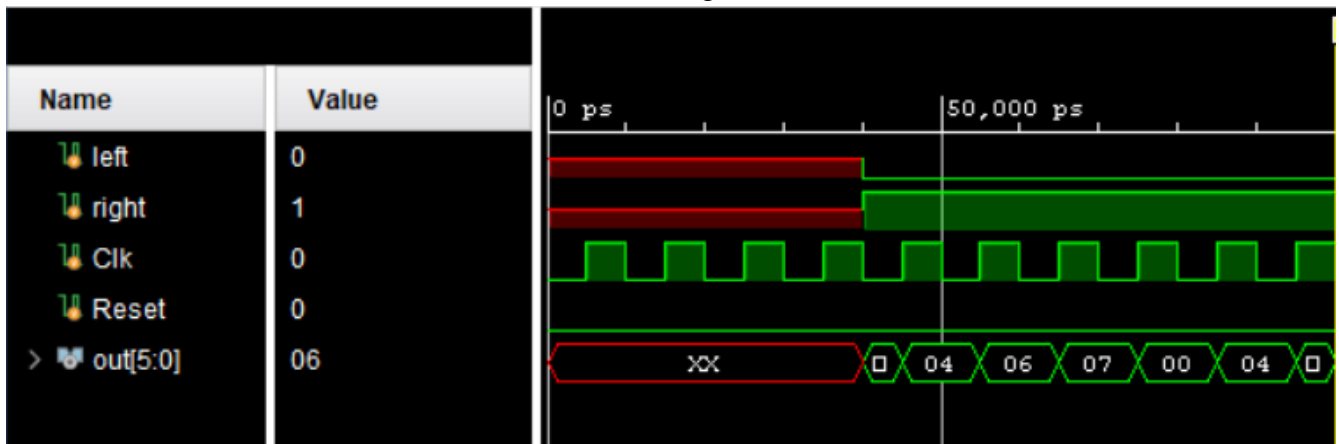
RIGHT TURN: 000100-4;000110-6;000111-7 (Put Right= 1 and Left=0 in the Test Bench)



4. Add clock division code to **Car_FSM.v** such that the actual input **Clk (Y9 pin with frequency of 100MHz)** is converted to Clock of frequency 2Hz. This 2Hz signal is used as clock for running the FSM.
5. Plan your I/O mapping (using **I/O planning** option) such that actual input **Clk** is connected to internal clock pin **Y9**, **Reset** is connected to push button switch, other inputs (**LEFT** and **RIGHT**) are connected to DIP switches and outputs are connected to LEDs. In the ZedBoard, the pin numbers indicating the DIP switches, LEDs and internal clock are listed in table uploaded in CMS. Save the mapping information as **Car_FSM.xdc**.
6. Synthesize (**Run Synthesis**).

Question: Paste the image showing the schematic after synthesis.


Answer:

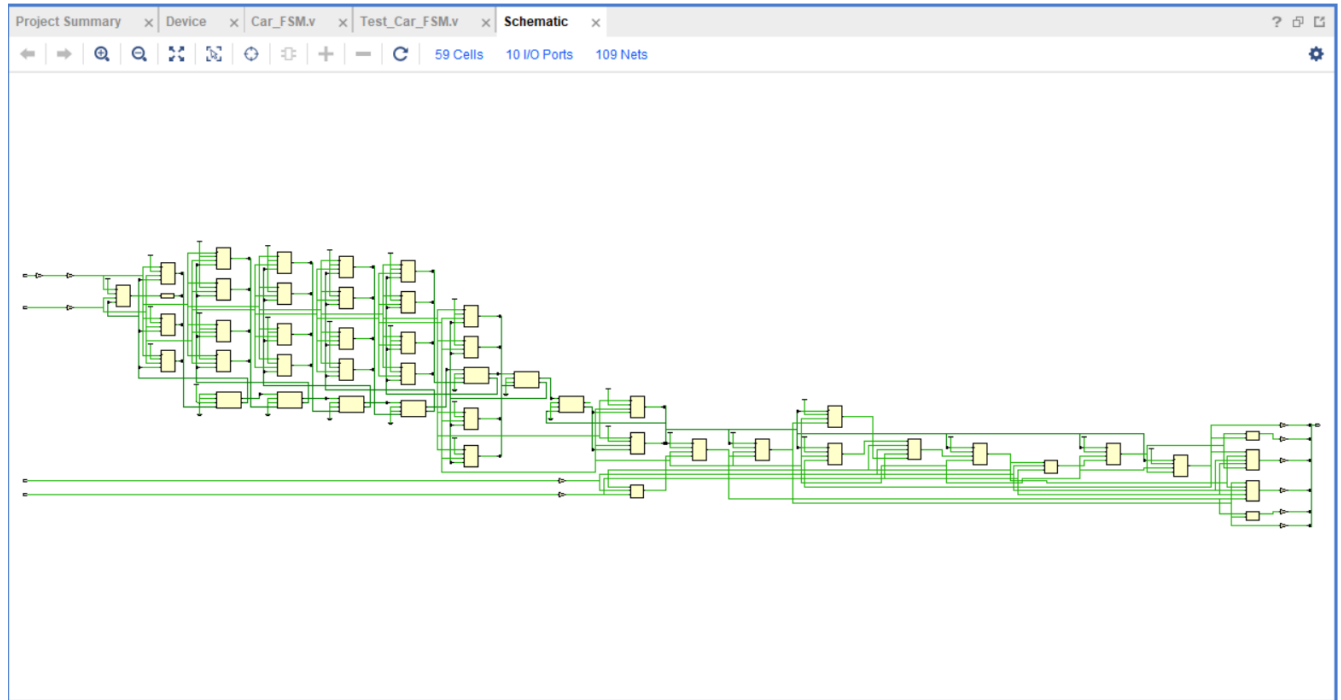

Question: Check the summary report and report hardware utilization for the FSM implementation.

Answer: Hardware Utilization=5+3.13+0.03+0.02=8.18%

Project name: lab5_6	
Project location: C:/Users/Lakshmi Mounika/lab5_6	
Product family: Zynq-7000	
Project part: xc7z020clg484-1	
Top module name: Car_FSM	
Target language: Verilog	
Simulator language: Mixed	
Synthesis	
Status:	Complete
Messages:	1 warning
Part:	xc7z020clg484-1
Strategy:	Vivado Synthesis Defaults
Report Strategy:	Vivado Synthesis Default Reports
DRC Violations	
Run Implementation to see DRC results	
Implementation	
Status:	Not started
Messages:	No errors or warnings
Part:	xc7z020clg484-1
Strategy:	Vivado Implementation Defaults
Report Strategy:	Vivado Implementation Default Reports
Incremental compile:	None
Timing	
Run Implementation to see timing results	

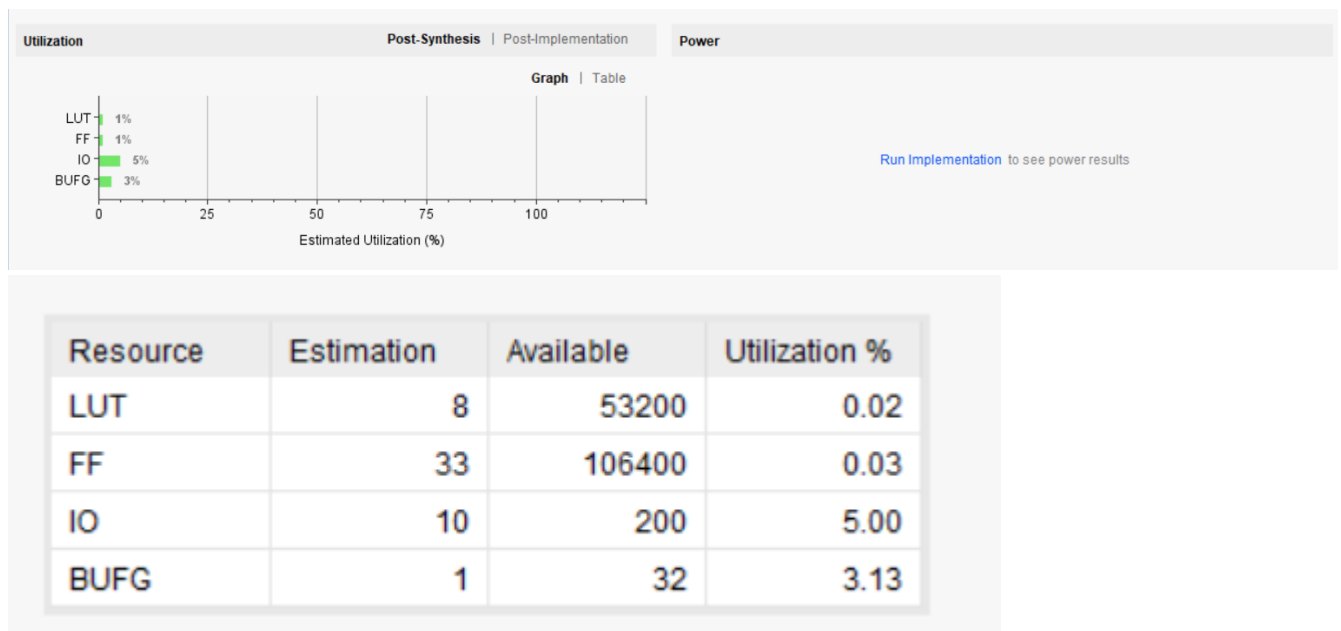

7. Implement the design (**Run Implementation**).
8. **Generate Bitstream** and port your design on to FPGA (**Open Hardware Manager**→ **New Target**→... **Program Device**)
9. Check the output on FPGA.
10. Show the output to the instructor.
11. Submit following files as a Zipped folder with file name as <Student1_ID_No>_<Name>.zip through CMS before due date.
 - 1) Completed Document
 - 2) Car_FSM.v (with proper comments)
 - 3) Test_Car_FSM.v (with proper comments)
 - 4) Car_FSM.xdc.
 - 5) Car_FSM.bit